

DARPA workshop presentation, 10/12/2021

Electronics for dense, efficient G-band arrays

Mark Rodwell


UCSB

rodwell@ece.ucsb.edu



100-300GHz wireless: applications

Short-range high-capacity wireless links (civilian infrastructure)

 ~300m range high-resolution imaging radar
concealed weapons detection
cars/drones in poor-visibility weather



Long-range, high-altitude links satellite-satellite, or air-satellite

  

The 100-300GHz 2D Array Challenge

Arrays can be made from either **tiles** or **trays**

Arrays might be vast: 100-1,000-10,000 elements

Arrays must be dense:


Many DC/IF/LO lines, plus antenna interface.
Fitting IC functions into available area.
Removing the heat.

IC density :




must fit PA, phase-shifter in $\sim(0.5\lambda)^2$.
0.68mm × 0.68 mm @ 220GHz.

Power and efficiency :

 high thermal load
high-efficiency PA at target ($\sim 200\text{mW}$) power





f	100	150	200	220	250	GHz
λ	3	2	1.5	1.36	1.2	mm
$\lambda/2$	1.5	1	0.75	0.68	0.6	mm

  
 


A simple 200GHz, $0.6\lambda \times 0.6\lambda$ array can just fit

Seo et al, 2021 IMS

 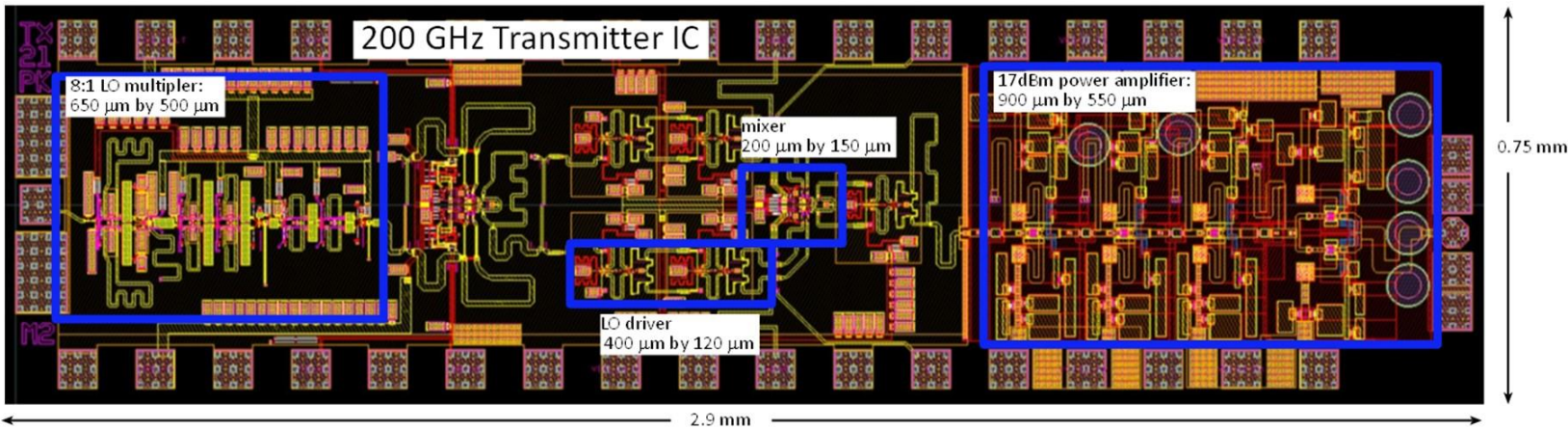

24-element array
4.5mm \times 4.5mm

  


Will a 220GHz dual-pol T/R array fit in $0.5\lambda \times 0.5\lambda$?

Substantially denser integration is needed.

All blocks must get smaller

 PA must get considerably smaller (seek 200mW, not 50mW)







Single-beam transmitter and receiver

Multi-beam transmitter and receiver

Single-beam dual-pol receiver+ transmitter

 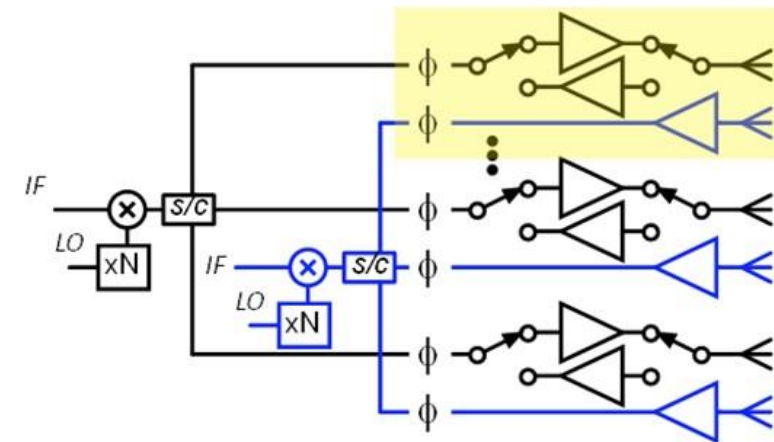  Multi-beam dual-pol receiver+ transmitter



Must increase IC density

Unlike CMOS, other mm-wave technologies are optimized for speed, not density

Transistors have been scaled for speed, but not always for density

FETs: small gate length, small gate-source, gate-drain spacings: fast

FETs: often large S/D pitch: low density



HBTs: small emitter widths, small base-collector junction widths: fast

HBTs: often large collector contacts and collector mesa: low density

Interconnects have been sized for low-loss 25-75 Ω lines, but not always for density

wide for desired 25-75 Ω Z_0 , low loss.

wide for high current-carrying (PAs)

  


PAs need fine-pitch interconnects: size, PAE

Allows dense multi-finger transistors

Within-cell wires are short: small parasitic inductances, capacitances

Because local impedances are high, capacitance is the main problem; **narrower is better.**

 Don't want 50Ω lines within multi-finger power transistor cell.



All transceiver blocks need fine-pitch interconnects

LO frequency multipliers, phase-shifters, LNAs, mixers, driver amplifiers

Controlled-impedance interconnects, and matching, between blocks



→ wide, lower-density interconnect

Short, random-impedance wires within blocks.

need fine-pitch wiring, small-footprint transistors

small inductive, capacitive wiring parasitics

wires need not be 50Ω → narrow → compact

  

Fine-pitched interconnects

CMOS and SiGe: interconnects above IC

lower planes: **dense**, random impedance
upper planes: **sparse**, controlled-impedance.

InP HBT: interconnects above IC





upper planes: **sparse**, controlled-impedance.
need to add **dense** interconnect layers
normal or inverted microstrip

Most mm-wave GaN : ground below IC, signal above IC

substrate microstrip.
lower-**density** interconnects.
minimum ground via spacings.

GaN with CMOS/InP-like wiring for denser interconnects ?

    dielectric loading \rightarrow increased C_{gs} , $C_{gd} \rightarrow$ decreased f_{τ} , f_{\max} **X**
substantial effect with FETs: (small g_m/W_g , small C/W_g)
minor effect with BJTs: (large g_m/W_g , small C/W_g)
Possible solution ? Air cavity above transistors



Need denser bypass capacitors

Not for small-value impedance-matching capacitors

high $C/A \rightarrow$ small dimensions \rightarrow large capacitance variability given normal linewidth variations

Application: RF bypass capacitors

goal: compact IC layouts, compact multi-finger power transistor cells







goal: avoid LC self-resonance. Need $\gg 220\text{GHz}$ (class A), $\gg 440\text{GHz}$ (class B)

Application: supply bypass capacitors

smaller bypass capacitors; with good bypassing, don't need differential stages for supply-related stability

Potential approach: replace 200nm Si_xN_y with $\sim 20\text{nm}$ ZrO_2 .

      $\sim 35:1$ smaller area for same capacitance



What sets DC power in mmWave ICs ?

$$P_{DC} = V_{DC} \times I_{DC}$$

Transistor is sized appropriately for the selected I_{DC} .

What size, what I_{DC} do we pick ?

Expected: device size, P_{DC} proportional to maximum RF output power

class-A PAs: $P_{RF} = (1/2)P_{DC}$.

Less required RF power \rightarrow less consumed DC power

Yet, we often cannot obtain this.

Impedance-matching sets minimum device size, minimum DC power




small-signal stages: optimum Z_s, Z_L tend to be proportional to $(1/g_m)$

small $I_{DC} \rightarrow$ small $g_m \rightarrow$ large optimum impedances, can't match !

Bipolar (SiGe, InP) transistors are attractive for low-power mmwave ICs

high g_m/I_{DC} ratio, $\sim 10:1$ better than FETs.

   high g_m per unit finger length; small transistor footprint



Efficient, small 220GHz PA: what do we need ?

Compact multi-finger transistor layouts

Efficient, compact on-wafer power-combining

Good transistor models: comprehensive measurements

Good power measurements calibrated to the IC pads

Load-pull measurements :

At 220GHz ?


Extrapolated from 94GHz ?

Current density, finger pitch limit cell output power

Electrode RC charging time $\propto (\text{finger length})^2$

Maximum finger length $\propto 1/\sqrt{\text{frequency}}$

 
Current per finger $\propto 1/\sqrt{\text{frequency}}$



Maximum cell width $\propto 1/\text{frequency}$

Maximum number fingers $\propto 1/\text{frequency}$

 Maximum current per cell $\propto 1/\text{frequency}^{3/2}$



Maximum RF power per cell $\propto (\text{maximum load resistance}) \cdot (\text{maximum current})^2 \propto 1/(\text{frequency})^3$


Compare to Johnson F.O.M.: maximum power per cell $\propto (\text{maximum voltage})^2 / (\text{minimum load resistance}) \propto 1/(\text{frequency})^2$

Current density, finger pitch limit cell output power

K. Shinohara, Teledyne: GaN HEMT thermal analysis


50Ω GaN PA cell @ 140GHz (1.6W)

 25V swing, 1.67mA/μm,
gates: 30 μm width, 15 μm pitch



50Ω InP HBT PA cell @ 280GHz (40mW)

 4V swing, 3.3mA/μm,
emitters: 6 μm length, 6 μm pitch



**High V_{br} , low I_{max} ? Device sized to drive 50Ω might approach $\lambda_g/4$ width.
Small finger pitch is critical; limited by thermal design**



Lower-loss corporate power-combiners

Wilkinson trees are lossy:

Signal passes through *many* 70.7Ω , $\lambda/4$ lines.

$\lambda/4$ lines are long.

  70.7Ω lines are narrow...and lossy \rightarrow **High loss.**




Single- $(\lambda/4)$ combiners are much less lossy

Each design uses a single *effective* $\lambda/4$ section.

Shorter lines, low- Z_0 lines \rightarrow lower loss

 But, low loss only if transistor cells fit.



Denser interconnects: improved PAE

Dense wiring: short lines: low loss


Smaller wiring pitch & capacitors

Smaller multi-finger footprint,

Shorter combiner lines

Less loss

Higher PAE.

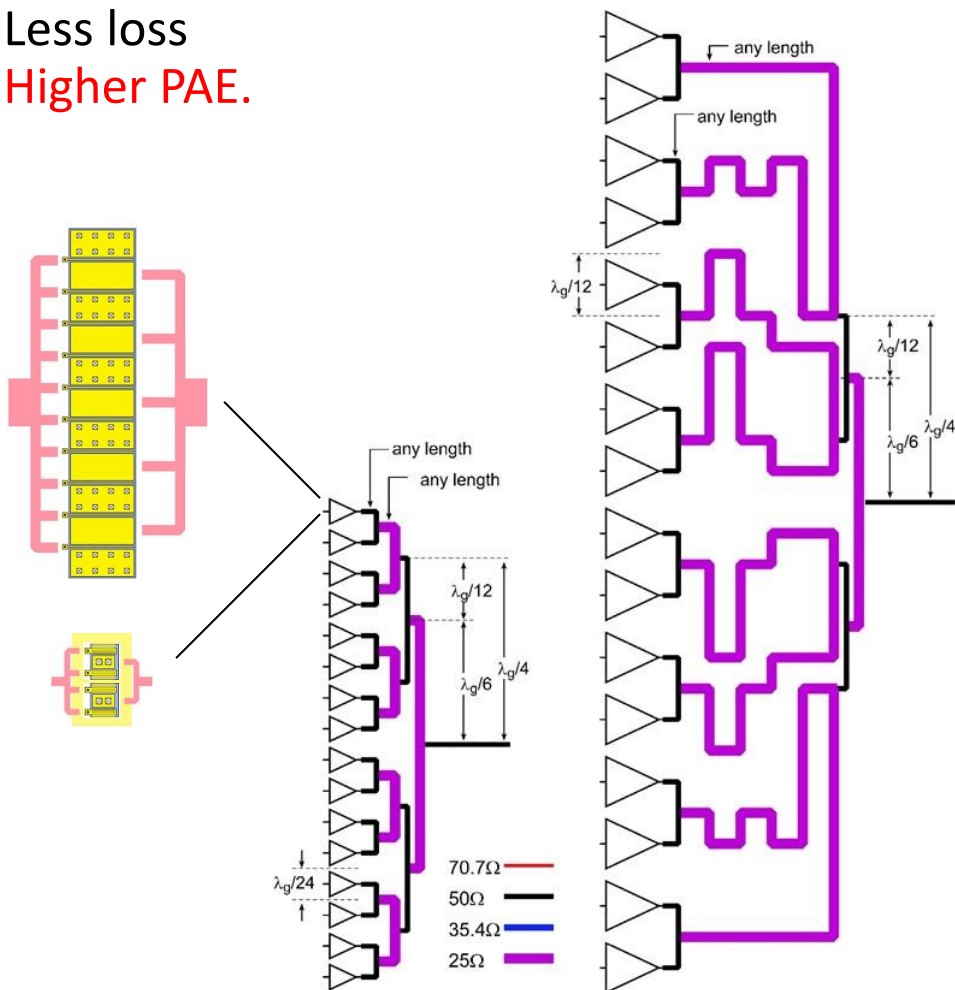


Present vs. desired IC density

$\lambda_g/24$ cell pitch: much smaller than in present ICs.

Need: smaller wiring pitch & capacitors, better heat removal.

 Some matching elements hard to fit: challenging layout.



Need accurate transistor models over full loadline

Observation: PA simulations strongly affected by details of saturation model

Static saturation (I-V collapse): **higher** simulated PAE

Dynamic saturation in **BJT's**: (Kirk effect: increased C_{cb} and increased τ_c): **lower** simulated PAE

Dynamic saturation in **FETs**: (back-injection: increased C_{gd} and increased τ_{ch}): **lower** simulated PAE





Implication: PA design needs accurate models over full signal swing.

Also: transit time and capacitance variations over (I,V) plane

Prescription: Develop accurate model over entire PA loadline

Over (I,V) plane: (a) measure S-parameters, (b) extract model at each bias point

    Fit to large-signal model over entire transistor safe operating area.



Extrapolate W-band load pull to 220GHz ?

Why not make W-band load-pull measurements, use these for 220GHz design ?

Large-signal effects, particularly saturation, can be **static**, **dynamic**, or both.

Example: HBT low-voltage limit, aka Kirk effect.

Decreased I_c , increased τ_c , increased C_{cb} .

All reduce the PA gain, all reduce the output power.

Can load pull tell you how much of each ?

Strong frequency variation of dynamic effects (τ_c , C_{cb})

No frequency variation of static effects (I_c)

FETs in saturation: similar mix of static, dynamic effects.

Extrapolating load-pull data to higher frequencies can thus be ambiguous.

Must model device self-heating

Observation: Good PA modeling at low V_{cc} , weaker modeling at high V_{cc} .

Inaccurate device model ? Unlikely: extensive characterization at foundry

More likely: transistor and IC self-heating



Need accurate temperature-dependent transistor electrical model

Need accurate model of device/IC self-heating

Dense IC: need good thermal management.

HBT self-heating observation

FETs show similar behavior

  

Power measurements calibrated to the IC pads

Present 220GHz PA characterization: scalar power correction

Output power measured using meter and waveguide-coupled wafer probe.

Probe loss corrected by 2-probe through-line measurement.

Does not correct for (S_{11} , S_{22}) of probe or power meter.


Does not ensure that PA load impedance is 50Ω (damaged/worn probe).

Alternative: power meter integrated with network-analyzer

NWA calibration moves reference plane to IC probe pad


Load impedance can be determined

 Adding E/H tuner: limited tuning of load impedance




Recent high-efficiency 100-300GHz PAs

 
Ahmed et al, 2020 IMS, 2020 EuMIC, 2021 IMS, 2021 RFIC
Teledyne 250nm InP HBT technology




140GHz, 20.5dBm, 20.8% PAE

 

130GHz, 200mW, 17.8% PAE

 

194GHz, 17.4dBm, 8.5% PAE

 

266GHz, 16.8dBm, 4.0% PAE

11.3% PAE, 17.0dBm at 190GHz

Teledyne 250nm InP HBT technology



Ahmed et al, unpublished

Simulated:


14% PAE, 17.5dBm at 210GHz

Measured:


11.3% PAE, 17.0dBm at 190GHz

  

(Used in 190-210GHz transmitter IC)

 

M. Seo et al, 2021 IMS

 

Feasibility of 220GHz, 200mW PA with 30% PAE

Design using TSC 250nm InP HBT model

2-stage, 22dB gain at saturation

transmission-line loss models fit to measurements.

→ 22% PAE at 200mW output power.

Approaches to reach 30% PAE.

Slightly adjusted transistor epi material.

Class B design.

end